



USN

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

21CS33

Third Semester B.E. Degree Examination, June/July 2024 Analog and Digital Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. With a neat circuit diagram and mathematical analyses explain voltage divider bias circuit. (10 Marks)
- b. With a neat circuit diagram explain the working of relaxation oscillator. (10 Marks)

OR

- 2 a. List the advantages of active filters over passive filters. (05 Marks)
- b. Explain any two performance parameters of power supply. (05 Marks)
- c. Explain R-2R ladder type D to A converter. (10 Marks)

Module-2

- 3 a. Simplify the following expression using K-Map and draw the logic circuit using basic gates.
 $F(A, B, C, D) = \sum m(7) + \sum d(10, 11, 12, 13, 14, 15)$. (10 Marks)
- b. Simplify the expression using Quine-McClusky method $F(A, B, C, D) = \sum m(0, 2, 3, 6, 7, 8, 10, 12, 13)$. (10 Marks)

OR

- 4 a. Using K-Map obtain SOP and POS expressions for
 $f(A, B, C, D) = \sum m(6, 8, 9, 10, 11, 12, 13, 14, 15)$. (10 Marks)
- b. With example explain,
 - i) Map-Entered variable method
 - ii) Petricks method. (10 Marks)

Module-3

- 5 a. What is Hazard? With example explain static-0 and static-1 Hazards. (10 Marks)
- b. Implement following function using 8:1 multiplexer:
 $f(a, b, c, d) = \sum m(0, 1, 5, 6, 8, 10, 12, 15)$. (10 Marks)

OR

- 6 a. Implement full adder using 3:8 decoder and NAND gates. (10 Marks)
- b. Design 7-segment decoder using PLA. (10 Marks)

Module-4

- 7 a. What are the 3 modeling styles in VHDL? Write VHDL code for full adder using structural model. (10 Marks)
- b. Derive the characteristics equations for D, T, SR and JK flip flops. (10 Marks)

OR

- 8 a. Draw the logic diagram of master slave JK flipflop using NAND gates and explain its working. (10 Marks)
- b. Explain the working of SR flipflop and show how it can be used in debounce circuit. (10 Marks)

Module-5

- 9 a. What is shift register? What are the different types of shift registers? Explain 8 bit serial-in serial-out shift register. (10 Marks)
- b. Explain the following: (10 Marks)
- i) Sequential Parity Checker
 - ii) Ring Counter.

OR

- 10 a. Design Mod-5 synchronous counter using JK flip flop. (10 Marks)
- b. With diagram explain parallel adder with accumulator. (10 Marks)
