



USN

--	--	--	--	--	--	--	--	--	--

18CS33

**Third Semester B.E. Degree Examination, June/July 2024**  
**Analog and Digital Electronics**

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

**Module-1**

- 1 a. Explain the construction working and characteristics of Light Emitting Diode. (06 Marks)
- b. With a neat circuit diagram and Mathematical analysis explain fixed bias circuit. (07 Marks)
- c. Show how IC-555 timer can be used as Astable Multivibrator with Waveforms. (07 Marks)

**OR**

- 2 a. Discuss successive approximation register method of A to D converter with detailed conversion process. (08 Marks)
- b. With neat diagram and waveform, explain working of inverting Schmitt trigger circuit. (06 Marks)
- c. Explain Adjustable Voltage Regulator with diagram and suitable equations. (06 Marks)

**Module-2**

- 3 a. Simplify the following function using K-map and obtain simplified Boolean expressions:  
 $f_1(a, b, c, d) = \sum m(0, 1, 2, 4, 5, 6, 8, 9, 10, 12, 13)$   
 $f_2(a, b, c, d) = \sum m(1, 3, 5, 7, 9) + \sum d(6, 12, 13)$ . (10 Marks)
- b. Simplify the following Boolean function by using Quine-Mcclusky (QM) method  
 $F(A, B, C, D) = \sum m(0, 2, 3, 6, 7, 8, 10, 12, 13)$ . Find all the prime implicants. (10 Marks)

**OR**

- 4 a. Minimize the following function using MEV technique, use 'd' a MEV variable  
 $f(A, B, C, D) = \sum m(0, 1, 2, 7, 8, 9, 14, 15)$ . (08 Marks)
- b. With an example, explain Petrik's method. (06 Marks)
- c. Solve the following clearly mention prime implicants and essential prime implicants  
 $f(a, b, c, d) = \sum m(1, 5, 6, 7, 11, 12, 13, 15)$ . (06 Marks)

**Module-3**

- 5 a. What are Hazards in digital systems? Explain static 1 and static – 0 hazards. (08 Marks)
- b. What is Multiplexer? Discuss 8 to 1 MUX with the help of logic diagram and equation. (06 Marks)
- c. Discuss the importance of three state buffer with example. (06 Marks)

**OR**

- 6 a. Show how using a 3 to 8 decoder and multiinput or gates following Boolean expressions can be realized simultaneously  
 $F_1(A, B, C) = \sum m(0, 4, 6)$   
 $F_2(A, B, C) = \sum m(0, 5)$   
 $F_3(A, B, C) = \sum m(1, 2, 3, 7)$  (06 Marks)
- b. Realize  $f(a, b, c, d) = \sum m(1, 5, 6, 10, 13, 14)$  using AND-OR logic with number of levels, Gates and Gate inputs. (06 Marks)
- c. Write a short note on PLA and PAL. (08 Marks)

**Module-4**

- 7 a. Discuss the operation of SR-Latch using NOR gates. Show how SR Latch can be used for switch debouncing. (08 Marks)  
b. Explain Gated SR-latch using NAND gate. (06 Marks)  
c. Differentiate between Latch and flip flop and explain the structure of VHDL program. (06 Marks)

**OR**

- 8 a. Explain the working operation of SR-flipflop and JK flip flop with truth table and waveforms. (08 Marks)  
b. Draw the logic diagram of master slave JK flip flop using NAND gates and explain the working with suitable timing diagram. (07 Marks)  
c. Discuss Toggle Flip Flop with truth table and characteristic equation. (05 Marks)

**Module-5**

- 9 a. Explain Parallel Adder with Accumulator with neat diagram and operation. (08 Marks)  
b. What is Register? Explain how 4 bit register with data load clear and clock constructed using D flip flops. (07 Marks)  
c. Discuss the operation of data transfer between Register. (05 Marks)

**OR**

- 10 a. Design the counter using D flip flop for the given sequence 0 – 3 – 2 – 6 – 4 – 7 – 0. (08 Marks)  
b. Explain synchronous Binary Counter with logical diagram and transition table. (06 Marks)  
c. Explain the working of 8 bit serial - in – serial - out shift register using SR flip flop. (06 Marks)

\* \* \* \* \*